

CS221: Digital Design

QM Logic Minimization

Dr. A. Sahu

Dept of Comp. Sc. & Engg.


Indian Institute of Technology Guwahati

Outline



- Study of Components
 - Logic Implementation Using MUX & Decoder
 - 4 Bit Adder, BCD adder
- Quine-McCluskey (QM) Logic Minimization
- Examples
- Writing C/C++ program for QM Method

Decoders

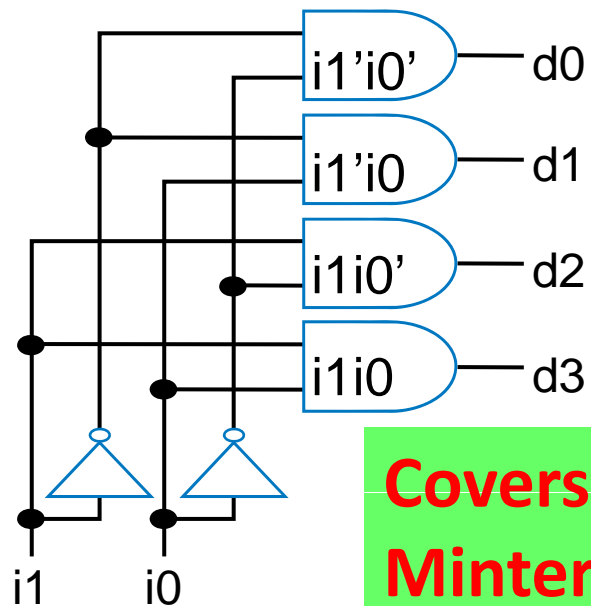- Internal design
 - AND gate for each output to detect input combination
- Decoder with enable e
 - Outputs all 0 if $e=0$, Regular behavior if $e=1$
- n -input decoder: 2^n outputs



**Covers All
Minterms**

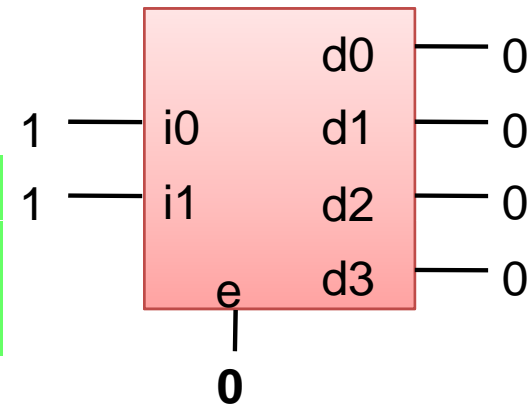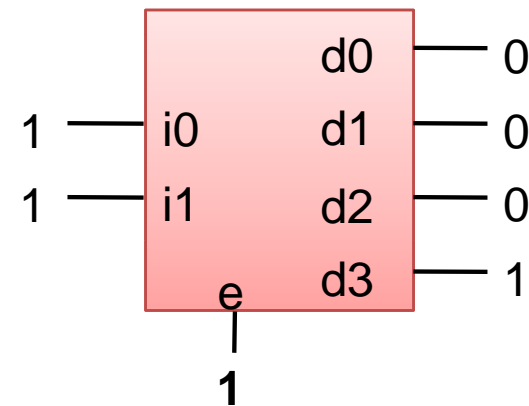

Boolean Function Implementation using Decoders

- Using a n -to- 2^n decoder and OR gates any functions of n variables can be implemented.



- Example:

$$S(x,y,z) = \Sigma(1,2,4,7) , \quad C(x,y,z) = \Sigma(3,5,6,7)$$

- Functions S and C can be implemented using a 3-to-8 decoder and two 4-input OR gates


Decoder: Covers All Minterms

Mux

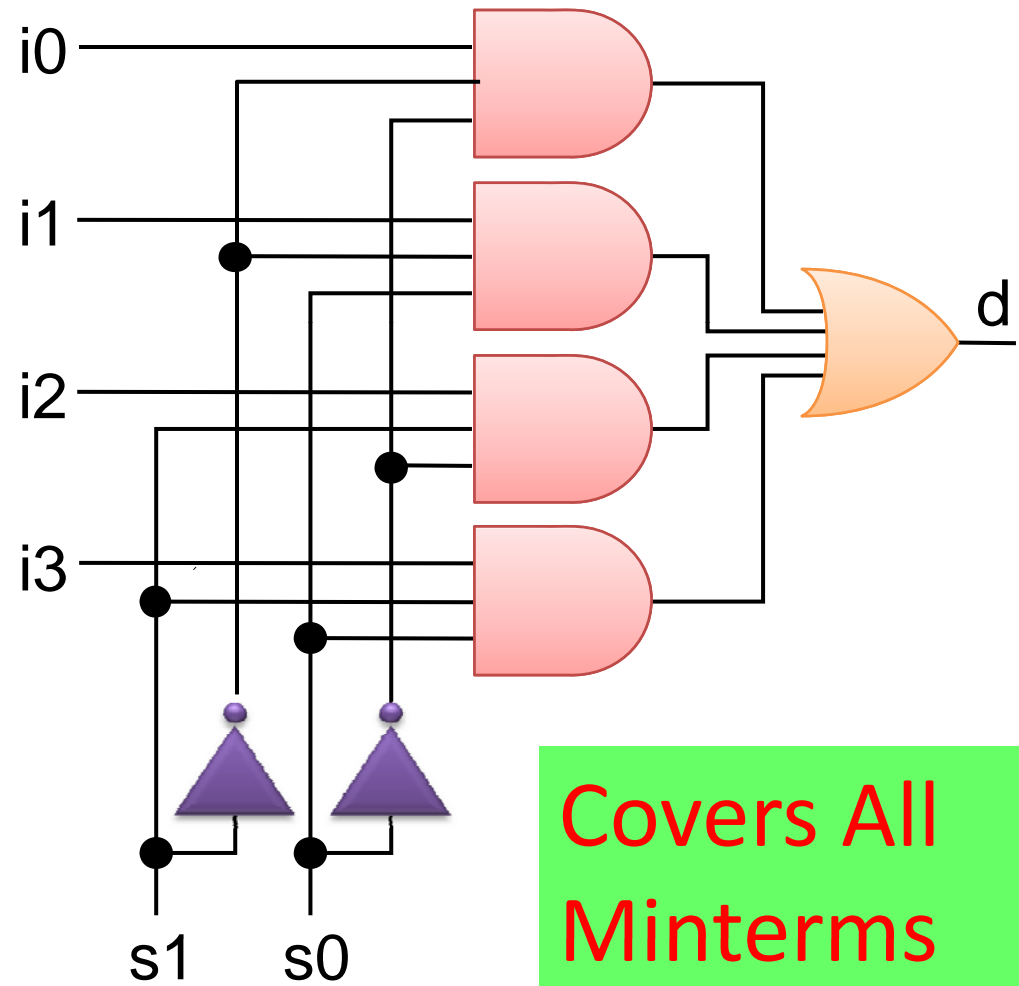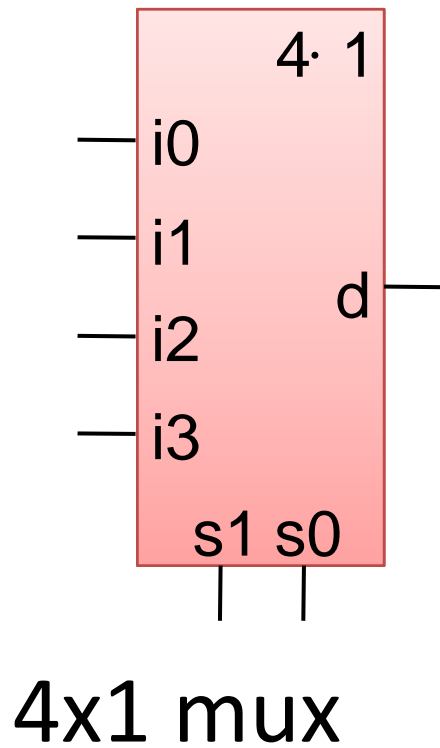


Covers All
Minterms

Implementing logic Function using MUX

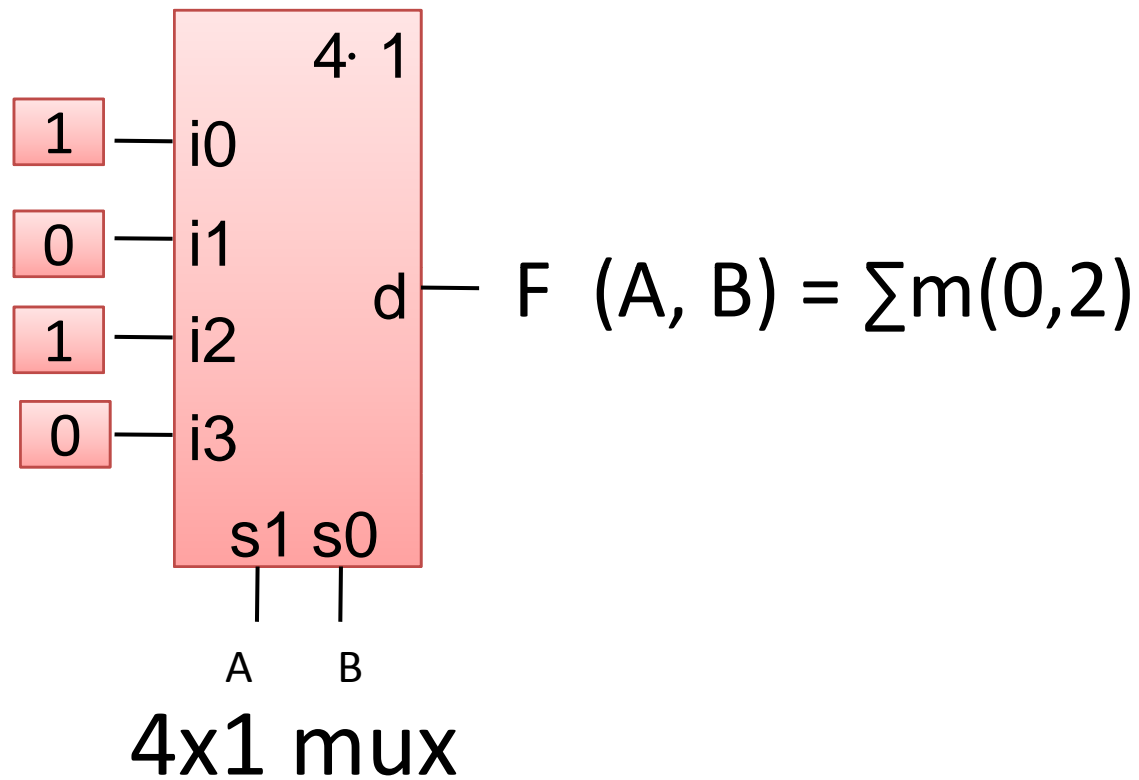


Adding Two One-bit Operands

- One-bit Half Adder:

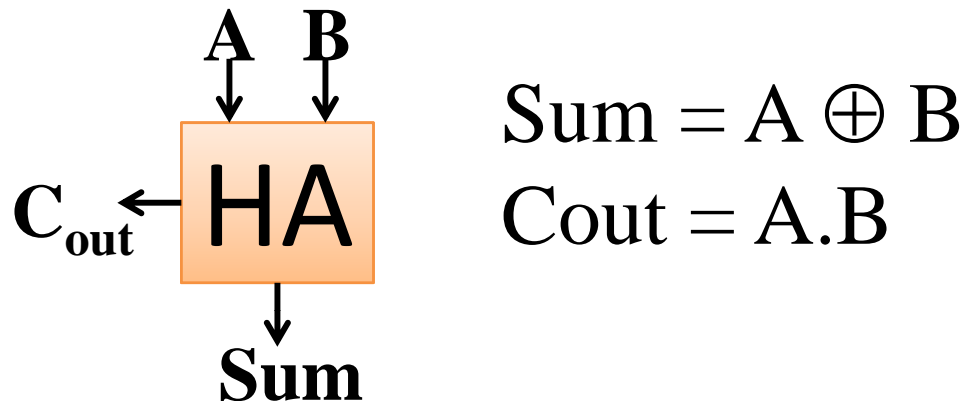

A	B	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


- One-bit Full Adder:

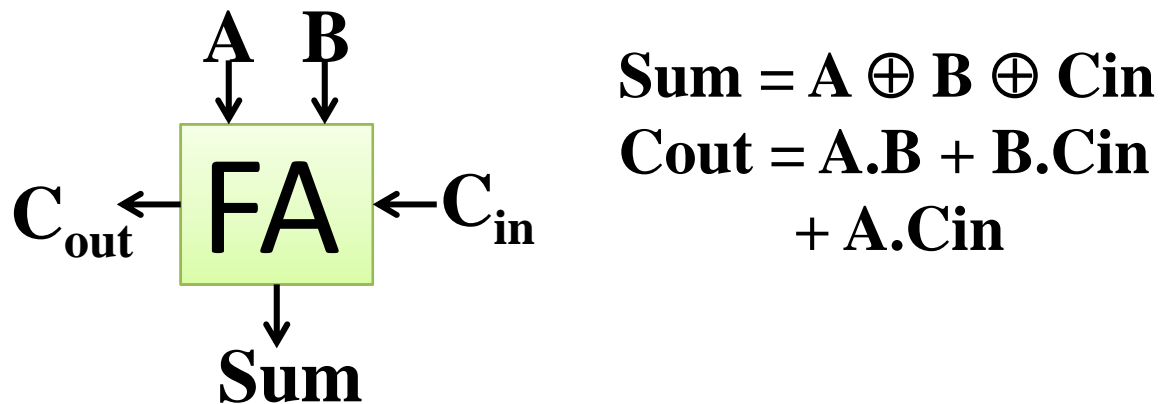


C _{in}	A	B	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

N-Bit Ripple-Carry Adder: Series of FA Cells


- To add two n-bit numbers

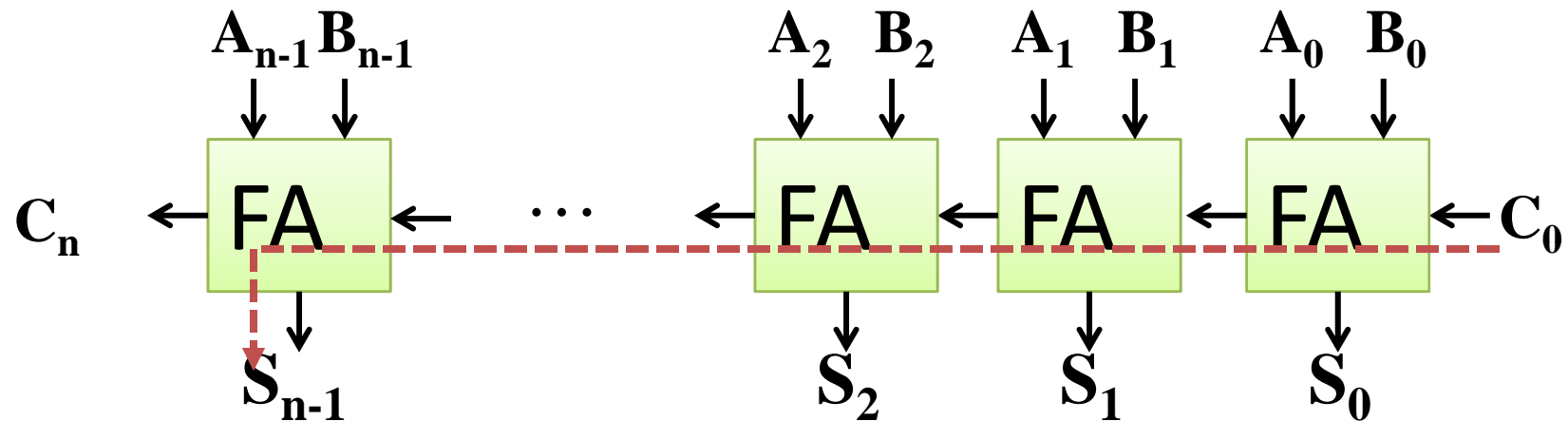

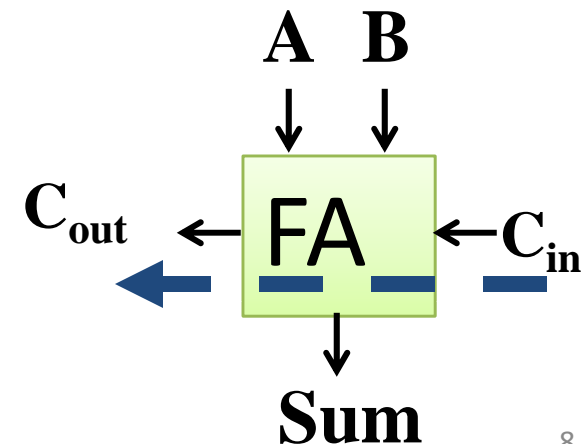- Adder delay = $T_c * n$
- $T_c = (C_{in} \text{ to } C_{out} \text{ delay})$ of a FA




4 bit Binary Adder

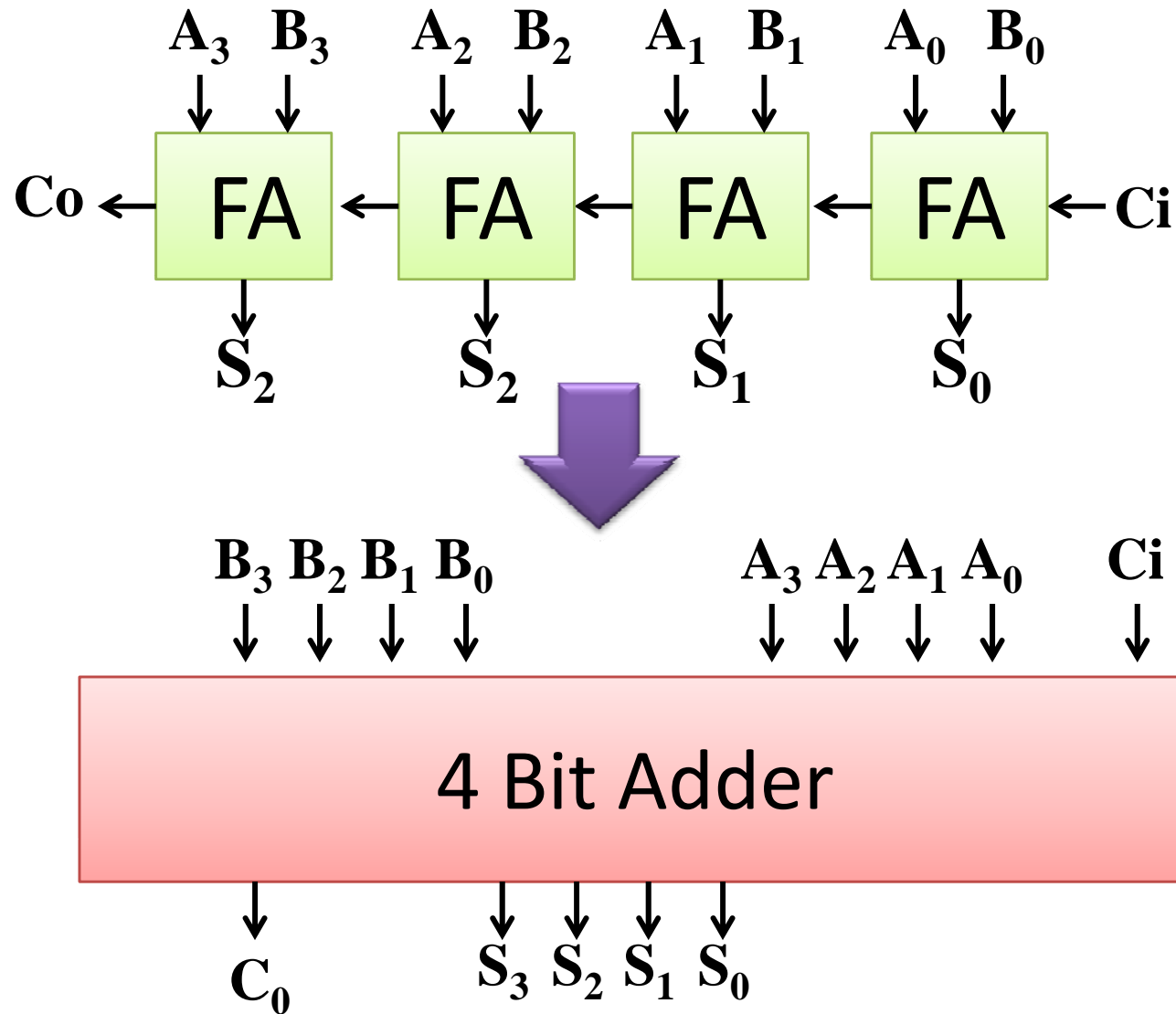

Binary Adder (Two Level)

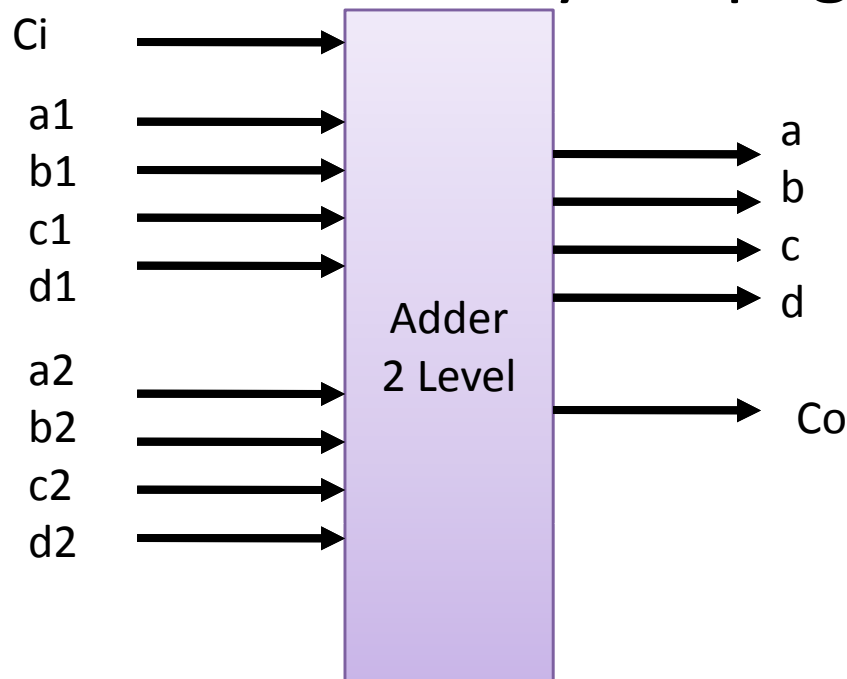
- Treat as 9 input & 5 output functions
- Generate Truth Table for each outputs
- Solve each function using KMAP/QM Method
- Only Two Level: No carry Propagation



Decimal Adder


- Decimal numbers are represented with BCD code.
- When two BCD digits A and B are added
 - if $A+B < 10$ result is a valid BCD digit
 - if $A+B > 9$ result will not be valid BCD digit. It must be corrected by adding 6 to the result
- If $A+B > 9$ add 6 to solve this issue

Decimal Adder

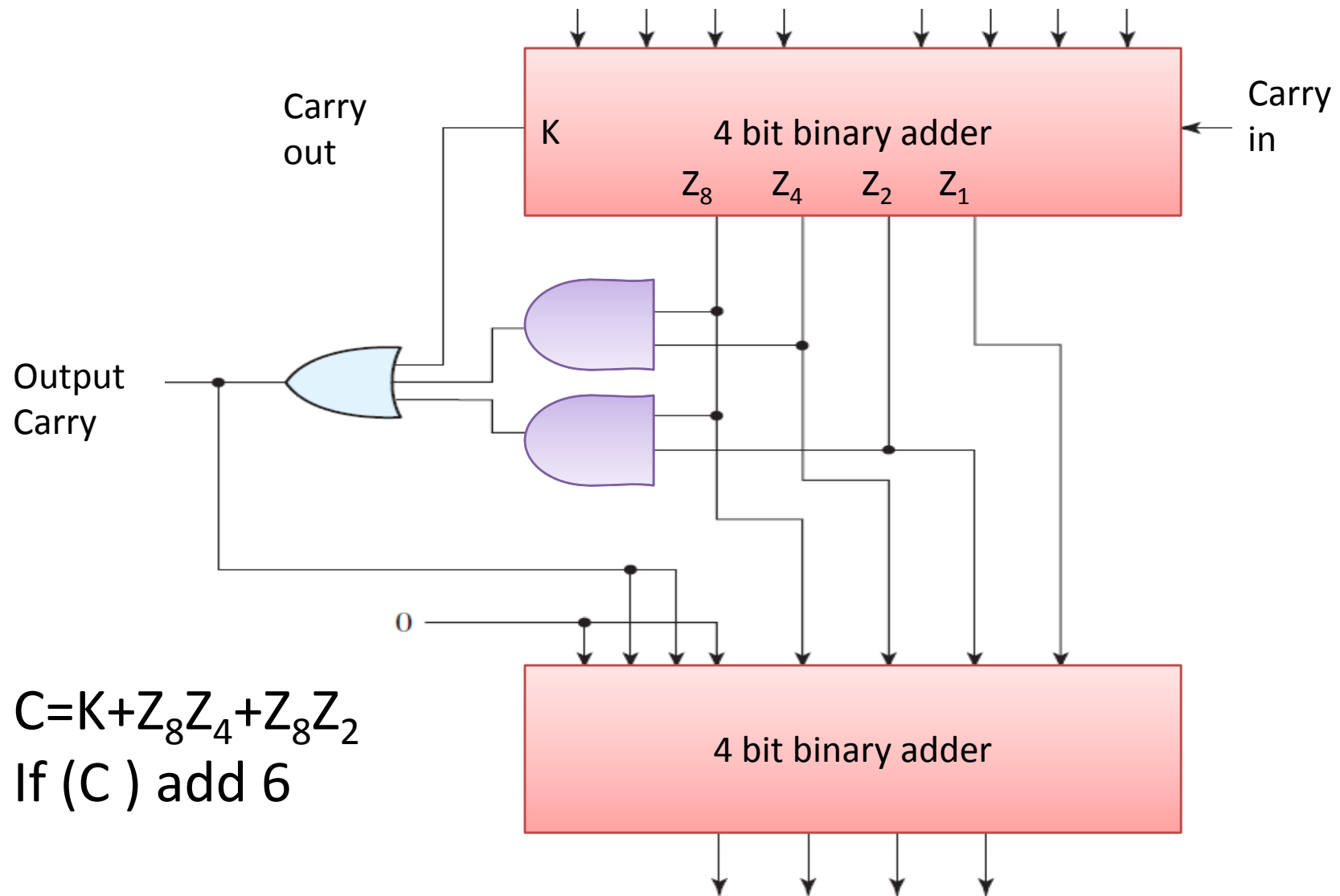

BCD Adder (Two Level)

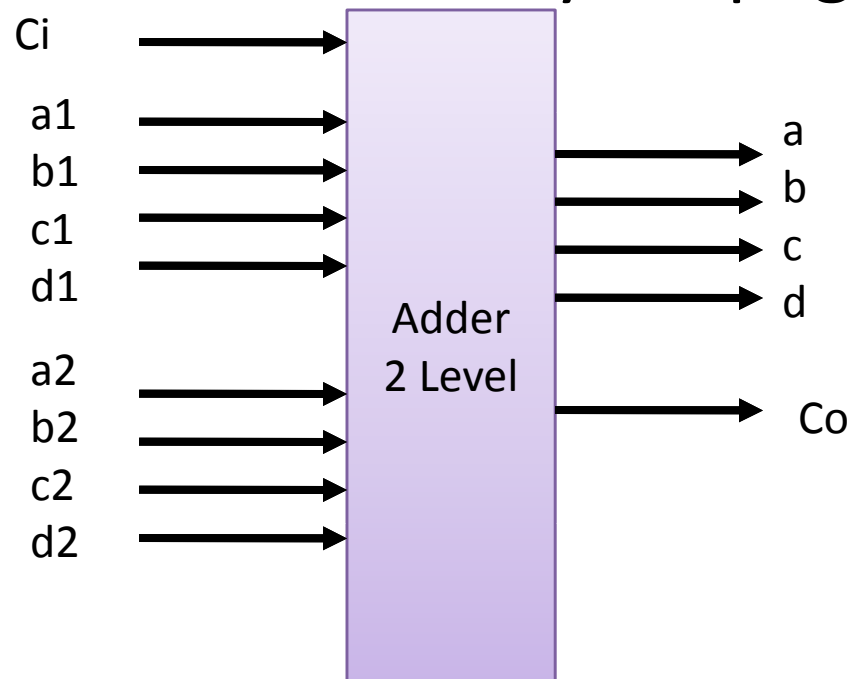- Treat as 9 input & 5 output functions
- Generate Truth Table for each outputs
- Solve each function using KMAP/QM Method
- Only Two Level: No carry Propagation



Quine-McCluskey Method for Minimization

- KMAP methods was practical for at most 6 variable functions
- Larger number of variables: need method that can be applied to computer based minimization
- **Quine-McCluskey** method
- For example:

$$\sum m(0,1,2,3,5,7,13,15)$$

QM Method

- Phase I : finding PIs
 - Tabular methods: Grouping and combining
- Phase II: Covers minimal PIs

QM Method

- Minterms that differ in one variable's value can be combined.
- Thus we list our minterms so that they are in groups with each group having the same number of 1s.
- So the first step is ordering the minterms according to their number of 1s (0-cube list)
- only minterms residing in adjacent groups have the chance to be combined.):

QM Method


$$\sum m(0,1,2,3,5,7,13,15)$$

0_Cube	
0	0000
1	0001
	0010
2	0011
	0101
3	0111
	1101
4	1111

QM Method: Combining Adjacent

- Compare minterms of a group with those of an adjacent one to form 1-cube list.
- When doing the combining, we put checkmark alongside the minterms in the 0-cube list that have been combined.


QM Method

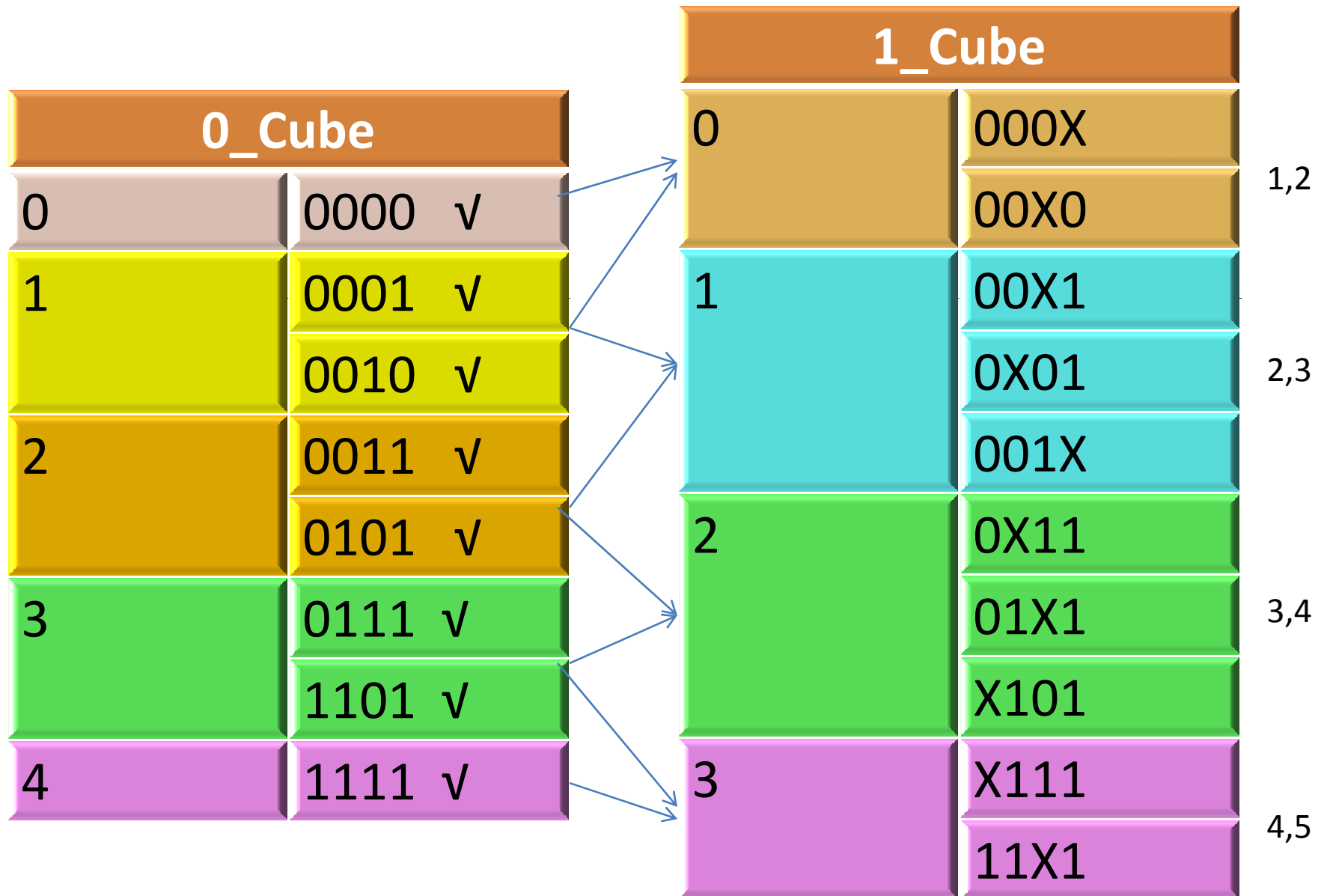

QM Method: Combining Adjacent

- Do same combination of comparing adjacent group minterms
 - To form 2-cubes, 3-cubes and so on.
- Only minterms of adjacent groups have the chance of being combined
 - **Which have an X in the same position.**

QM Method

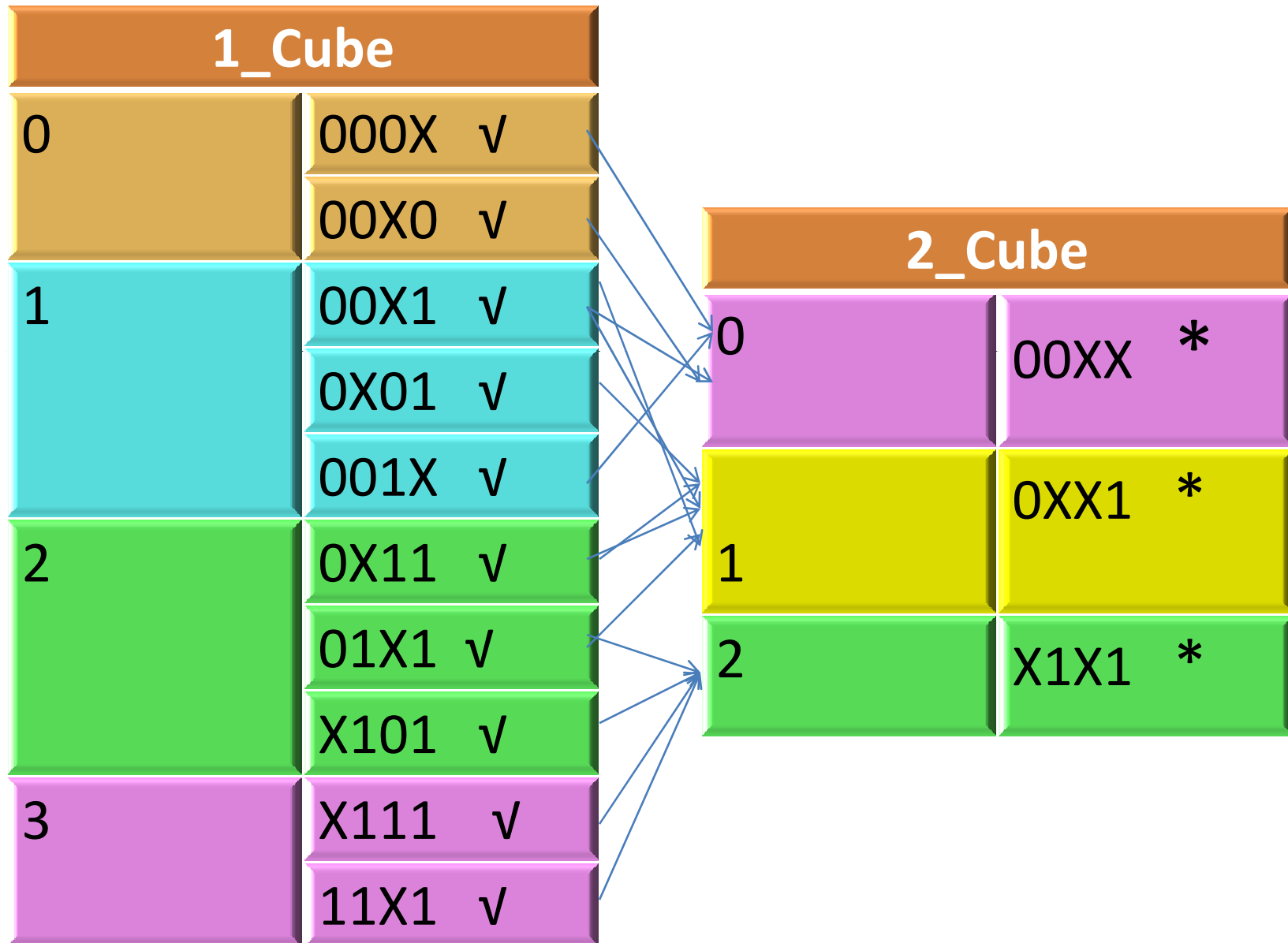

Q-M Method: Cover Pls

- Pls : terms left without checkmarks.
- After identifying our Pls, we list them against the minterms needed to be covered

$$\sum m(0,1,2,3,5,7,13,15)$$

	0 0 0 0	0 0 0 1	0 0 1 0	0 0 1 1	0 1 0 1	0 1 1 1	1 1 0 1	1 1 1 1
0 0 x x	✓	✓	✓	✓	✓	✓		
0 x x 1		✓	✓	✓	✓	✓		
x 1 x 1					✓	✓	✓	✓
Func	✓	✓	✓	✓	✓	✓	✓	✓

QM Method : Covers

- To find a minimal cover, we first need to find essential PIs
- To do this we need to find columns that only have one checkmark in them, the according row will thus show the essential PI.
- After identifying essential PIs, that are necessarily part of the cover, we cover any remaining minterms using a minimal set of PIs.

In this example: $F(a,b,c,d) = \overline{\overline{a}}\overline{\overline{b}} + bd$

Thanks